

PHYS 605 Lab #7

Morgan A. Daly and Evin O'Shea
(Dated: April 6, 2016)

I. INTRODUCTION AND THEORY

A. Purpose

The goal of part A of the lab was to investigate the internal resistance of the protoboard's AC voltage supply. This was a good practice in measuring the output voltage and output impedance of a circuit.

Part A of the lab gave practice for part B of the lab which was to investigate the output impedance of an op amp circuit. In this case the circuit was an inverting amplifier with a gain of three. Along with output impedance, the limitations of possible loads and the affects of different resistor values in the op amp circuit.

Part C of the lab was to build a different op amp circuit. The lab group chose to build a high pass filter and amplifier. This circuit's nature was investigated by measuring output voltage versus input frequency. The plot of this relationship will show the nature of the filter.

B. Background / Theory

Output impedance and voltage of a circuit is important to know. When a voltage is being supplied from an active circuit to a load, the output impedance can tell a lot about the limitations of the loads that can be used. If the output impedance of a passive circuit is much higher than the impedance of the circuit load, then sag can occur. This will mean that the circuit will not work as desired. The magnitude of the output impedance of a circuit can be measured by measuring the output voltage of a circuit with no load, and then measuring the output voltage with a load. The output impedance in voltage can be described by the thevenin equivalent of the circuit. The thevenin voltage is measured when the output voltage is measured without the load. When the load is applied, knowing the load resistance and the voltage across the load will give the norton current. Together, the thevenin voltage and norton current can give the output impedance. A diagram of the circuit used to make measurements that will allow the norton current to be calculated is shown below:

This type of measurement can be made on any circuit. For the second part of the lab, the same set up can be used where V_o and R_o are the output voltage and output impedance of the circuit created for the second part of the lab.

Op amps are active circuit elements that can be used in a multitude of ways. The most important property of an op amp is that the positive and negative terminals of the op amp will be equal. This means that since the

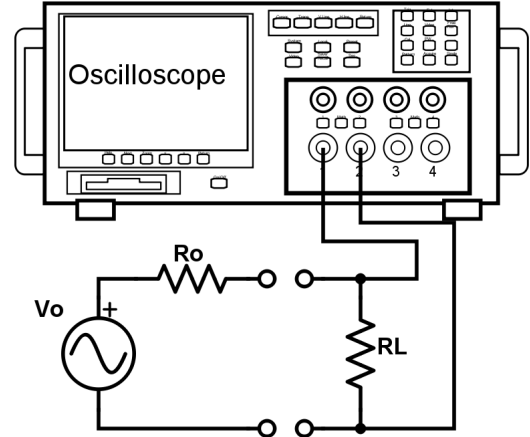


FIG. 1: This circuit is designed to discover the norton current with can give rise to R_o if V_o is measured separately.

positive terminal is grounded, the voltage of the positive and negative terminal will both be zero. This means that $\frac{V_{in}}{R_{in}} = -\frac{V_{out}}{R_F}$. Given the definition of the gain we obtain:

$$gain = \frac{V_{out}}{V_{in}} = -\frac{R_F}{R_{in}} \quad (1)$$

The inverting amplifier built for this lab is shown below:

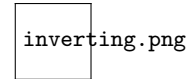


FIG. 2: This circuit is both a high pass filter and an amplifier.

For the third part of the lab, a high pass filter and amplifier was made with the op amp. This circuit is shown below. This circuit is a high pass filter because the capacitor only allows high frequency voltages to pass through. In a DC circuit, a capacitor will simply be charged and no current will flow after. In an AC circuit, changes in the voltage across the capacitor on one side will cause changes in voltage on the other side. This will allow the AC current to flow through the capacitor. Since the capacitor responds to changes in voltage, higher frequency voltages will pass through the circuit more easily than low frequency voltages. This is the reason that a circuit in this situation will act as a high pass filter. In this circuit, since there is a negative feedback, the positive and negative terminals of the op amp will have an equal voltage. Again, since the positive terminal is grounded, the

voltage of the positive and negative terminal will both be zero. Again the gain of this circuit will be determined by:

$$gain = -\frac{Z_F}{Z_{in}} \quad (2)$$

This time however, these are complex imedances. In this case, $Z_{in} = R_{in} + C_{in}$. The magnitude of this gain will depend on the frequency of the input voltage. The filter will allow high frequency voltages to pass and low frequencies will have a gain of less than one. The characteristic frequency of an RC circuit is given below:

$$\omega_{RC} = \frac{1}{R\omega} \quad (3)$$

The op amp circuit built for this part of the lab is shown below:

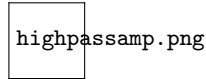


FIG. 3: This circuit is both a high pass filter and an amplifier.

II. METHODOLOGY

1. Connect the oscilloscope directly to the Protoboard AC voltage supply and mneasure the output voltage.
2. Set up the circuit shown in figure (1) record the voltage across the resistor and record the resistor value
3. Build the op amp circuit from figure (2).
4. Take record of the output voltage with no load at-tatched.
5. Add a load to the circuit with a large value as to emilinate sag.
6. Measure the voltage across the load resistor and the value of this resistor.
7. Change the frequency and take nots on any changes in the plot on the oscilloscope.
8. Change the load resistor and investigate the limi-tations fo the circuit.
9. Build the circuit from figure (3).
10. Take recordings of output voltage as the frequency is varied and the input voltage is kept constant.

III. RESULTS AND ANALYSIS

A. Data

The half wave rectifier was investigated with various input voltages and frequencies. All voltages for V_{in} and V_{out} were maximum voltages.

The input source was initially set to an amplitude of 2.64V and frequency 7.225Hz. The V_{out} measured across the diode was 1.80V.

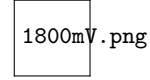


FIG. 4: $V_{in} = 2.64V$, $f = 7.225Hz$, $V_{out} = 1.80V$

For part C of the lab the group built a high pass filter and amplifier circuit using the op amp. The input voltage used for this section was 1V peak-to-peak. The data recorded is shown below:

frequency (Hz)	V_{out} (V)
102000	1.76
92590	1.84
58140	1.92
2119	1.88
1000	1.64
735.3	1.46
457.8	1.16
102	0.324
52.63	0.168
10.75	0.044

B. Calculations

For Part C of the lab, the gain of the op amp unit is: $gain = \frac{V_{out}}{V_{in}}$ The calculated data for this part of the lab is shown below:

frequency (Hz)	gain (dB)
102000	4.91
92590	5.30
58140	5.67
2119	5.48
1000	4.30
735.3	3.29
457.8	1.29
102	-9.80
52.63	-15.5
10.75	-27.1

C. Analysis

For part C of the lab the group built a high pass filter and amplifier circuit using the op amp. For this circuit, a bode plot can be made to shown the nature of the filter. This plot is shown below.

At the characteristic frequency, ω_{RC} the gain is 0dB which is what was expected. The plot demonstrates that the gain in dB is negative for the frequencies

below ω_{RC} and is positive for frequencies above ω_{RC} . This means that the low frequencies are filtered and the high frequencies are passed through the filter. This is the exact nature expected for a high pass filter.

IV. CONCLUSION